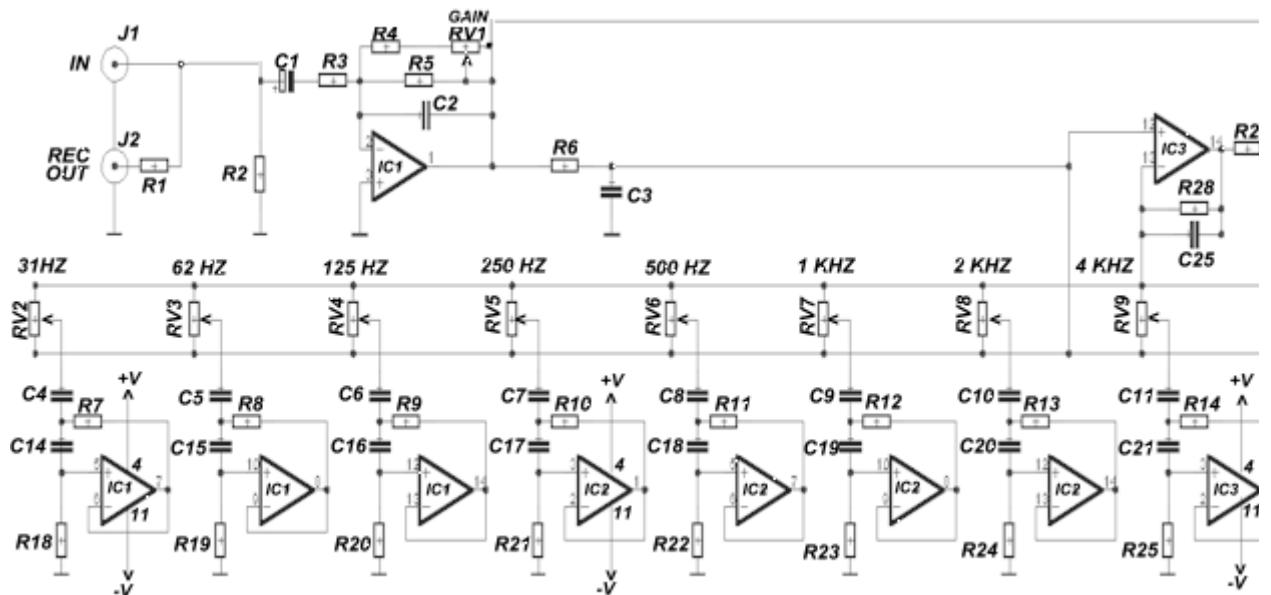


10 Band Graphic Equalizer (1)



Graphic Equalizer 10 - Band

**Click on the Image for its larger version

With graphic equalizer we make selective cutting off or boost, of selected departments of acoustic spectrum. With this way we can adapt the musical reproduction, in the characteristics of space where we hear. This can create however also problems if go to far specifically in the gain of some area, with result the distortion. The circuit should be made in two pieces, one for each channel, the potesometer regulation it should they are Fader. With switch S1 we can by pass the circuit, leaving the musical program, to pass without alteration (FLAT). With the potesometer RV1 we regulate the gain of each channel.

**ФЕЧНИКБ
ЧБСБКФЗСЙУФЙКБ
РСПФХРПХ -PROTOTYPE
SPECIFICATIONS**

Бръксийуз ухчныфзфбт - Frequency Response	103Ж - 30 К3Ж ±0.5db
Сэимийуз кЭсдпхт квие ресайпчЮт - Adjust Gain for each band	±12 dB
Сэимийуз кЭсдпхт - Adjust Gain for each Channel	- 9db to +14db
S/N	82db
Рбсбмъсцщуз (FLAT) - Т.Н.Д	0.03%
Уэниефз бнфяуфбуз ейуьдпх - Input Impedance	47КЩ
Уэниефз бнфяуфбуз еоьдпх - Output Impedance	100Щ
Фспцпдпуяб - Power Supply	±15V dc / 300 mA

Part List

R1-29=100 ohms	C7=220nF 100V	C20=1nF 100V
R2-5-31=1Mohms	C8=100nF 100V	C21=560pF
R3=47Kohms	C9=47nF 100V	C22=270pF
R4=15Kohms	C10=27nF 100V	C23=150pF

R6-28=10Kohms	C11=12nF 100V	C25=150pF
R7....17=1Kohms	C12=6.8nF 100V	C26=10uF/25V
R18....27=220Kohms	C13=3.3nF 100V	RV1=250Kohms Lin.
C1=47uF/25V	C14=68nF 100V	RV2.....12=4.7Kohms Lin.
C2=47pF	C15=33nF 100V	IC1...3= TL074
C3=150pF	C16=18nF 100V	S1=2X2 SW
C4=1.5uF 100V	C17=8.2nF 100V	J1...3=RCA Jack
C5=820nF 100V	C18=3.9nF 100V	All Resistors is 1/4W 1%
C6=390nF 100V	C19=2.2nF 100V	