

Walky-talky in this website is world 1st verified walky-talky project without using coil. Walky talky is very interesting and attain grabbing project for electronics hobbyist. Communication is done without any physical connection and mobile network up range of 500 meter. Almost all communication devices utilize coil which is burden for electronics hobbyist. So, we design this circuit without using any coil.

Circuit Descriptions of walky-talky

The entire circuit of walky-talky is divided into two main section transmitter and receiver section.

Transmitter section:- Transmitter section utilize IC NE566 (IC₄) as VCO (Voltage Control Oscillator) for generating frequency about 30 KHz.

Resistor R₂₄ with Capacitor C₂₄ used as frequency components for frequencies determination. Voice is pick-up by mike (MIC₁) and changed it into equivalent electrical signal. Signal from microphone is amplified by transistor T₄ and given to pin no 5 of IC₄. NAND gate N₁ with crystal oscillator XT₄ finalizes the output from pin 3 of IC₃. Lastly, signal from

NAND N_2 through N_3 and N_4 given to antenna for transmission.

Receiver section: – Transmitted signal from another walky-talky is received from same antenna which is used for transmission. Field effect transistor T_1 boosts the received signal and make more powerful and send to amplifier section made from transistor T_2 and T_3 with crystal oscillator XT_1 through XT_3 . Detector section is made from diode D_1 , Capacitor C_6 and resistor R_{12} . 30 KHz frequency is obtained from detector section.

Frequency of Phase Locked Loop IC NE565 (IC_1) is adjusted by capacitor C_9 , resistor R_{17} and variable resistor VR_1 . Amplifier IC LM386 (IC_2) is used to amplify the signal and given to speaker.

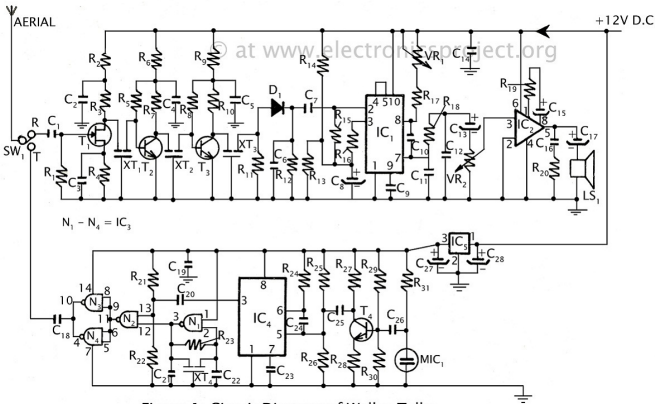


Figure 1: Circuit Diagram of Walky-Talky

PARTS LIST

Resistors (all ¼-watt, ± 5% Carbon)

$R_1 = 47 \text{ K}\Omega$

$R_2 = 100 \Omega$

$R_3, R_4, R_{11}, R_{27} = 2.2 \text{ K}\Omega$

$R_5 = 330 \text{ K}\Omega$

$R_6, R_{10} = 560 \Omega$

$R_7 = 1 \text{ K}\Omega$

$R_8 = 220 \text{ K}\Omega$

$R_9 = 100 \Omega$

$R_{12}, R_{15}, R_{16} = 4.7 \text{ K}\Omega$

$R_{13}, R_{31} = 10 \text{ K}\Omega$

$R_{14} = 15 \text{ K}\Omega$

$R_{17} = 1.8 \text{ K}\Omega$

$R_{18} = 1.2 \text{ K}\Omega$

$R_{19} = 1 \text{ K}\Omega$

$R_{20} = 4.7 \Omega$

$R_{21}, R_{22} = 100 \text{ K}\Omega$

$R_{23} = 120 \text{ K}\Omega$

$R_{24} = 5.6 \text{ K}\Omega$

$$R_{25} = 22 \text{ K}\Omega$$

$$R_{26} = 150 \text{ K}\Omega$$

$$R_{28} = 330 \Omega$$

$$R_{29} = 220 \text{ K}\Omega$$

$$R_{30} = 47 \text{ K}\Omega$$

$$VR_1 = 4.7 \text{ K}\Omega$$

$$VR_2 = 22 \text{ K}\Omega$$

Capacitors

Wideband Antenna Shop

High-end Wideband &
Broadband Antennas, 1Hz to
40GHz



$$C_1, C_6, C_{10}, C_{24} = 1 \text{ KpF}$$

$$C_2, C_4, C_5 = 47 \text{ KpF}$$

$$C_3 = 20 \text{ KpF}$$

$$C_7, C_9, C_{23} = 2.2 \text{ KpF}$$

$$C_8 = 4.7 \mu\text{F}/16\text{V}$$

$$C_{11} = 22 \text{ KpF}$$

$$C_{12}, C_{16} = 0.1 \mu\text{F}$$

$$C_{13} = 2.2 \mu\text{F}/16 \text{ V}$$

$$C_{14}, C_{19}, C_{25}, C_{26} = 0.22 \mu\text{F}$$

$$C_{15} = 10 \mu\text{F}/16\text{V}$$

$$C_{17} = 220 \mu\text{F}/16\text{V}$$

$$C_{18}, C_{20} = 10 \text{ KpF}$$

$$C_{21}, C_{22} = 68 \text{ pF}$$

$$C_{27} = 1000 \mu\text{F}/16\text{V}$$

$$C_{28} = 10 \mu\text{F}/16\text{V}$$

Semiconductors

$$IC_1 = \text{NE565 (Phase Lock IC)}$$

$$IC_2 = \text{LM386 (Amplifier IC)}$$

$$IC_3 = \text{CD4011 (Quad 2-input NAND Gate IC)}$$

$$IC_4 = \text{LM566 (Voltage Controlled Oscillator)}$$

$$IC_5 = \text{LM7812 (Voltage Regulator)}$$

$$T_1 = \text{BFW10}$$

$T_2, T_3 = \text{BF194}$

$T_4 = \text{BC148}$

$D_1 = \text{1N4148}$

Miscellaneous

$XT_1 - XT_4 = 10.7 \text{ MHz crystal}$

$SW_1 = \text{Single pole double throw switch}$

$LS_1 = 8\Omega \text{ speaker}$

$MIC_1 = \text{Condenser microphone}$

Areal